
Building Altoids Flashlight Workshop

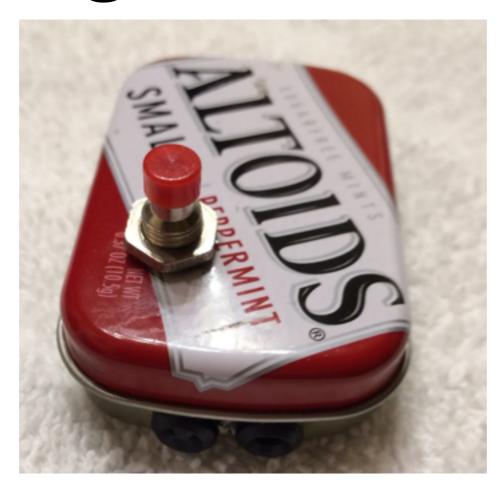

Christopher & Blake Judd

Why build a flashlight?

learn basic electronics













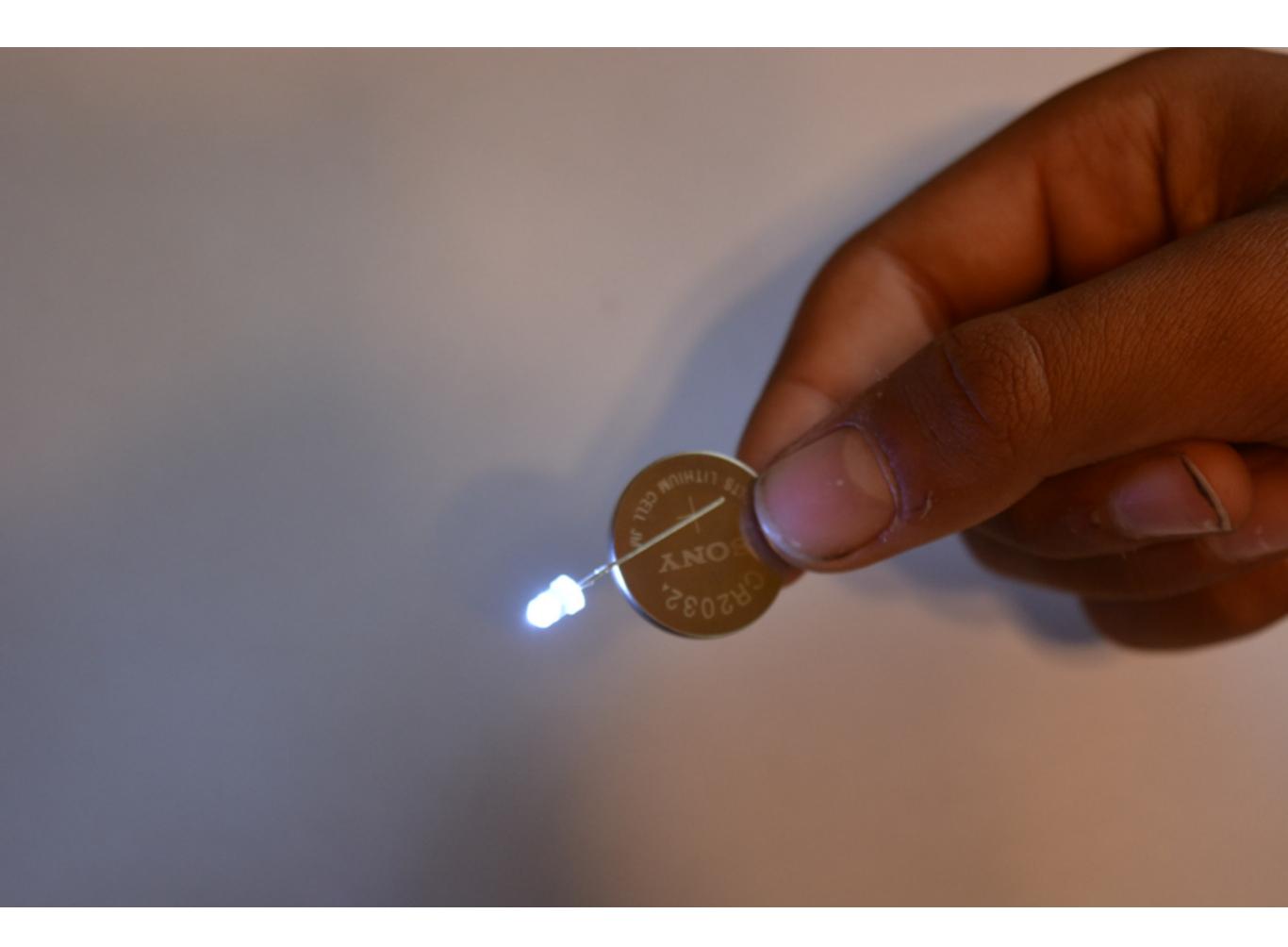








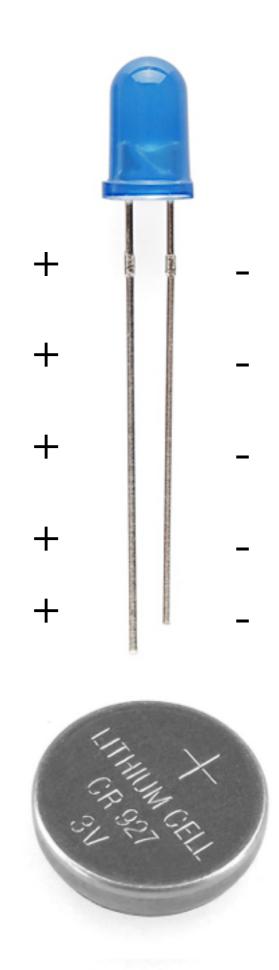





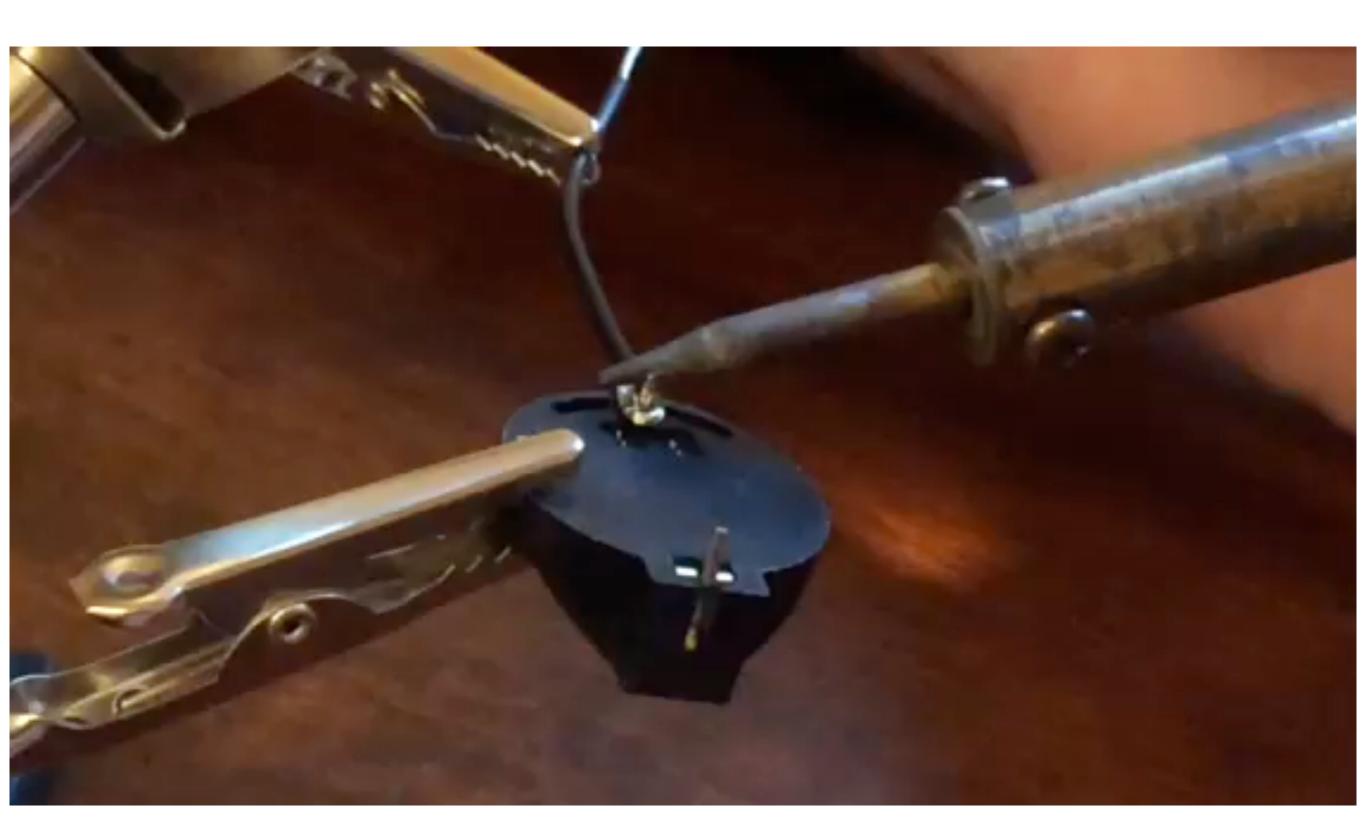

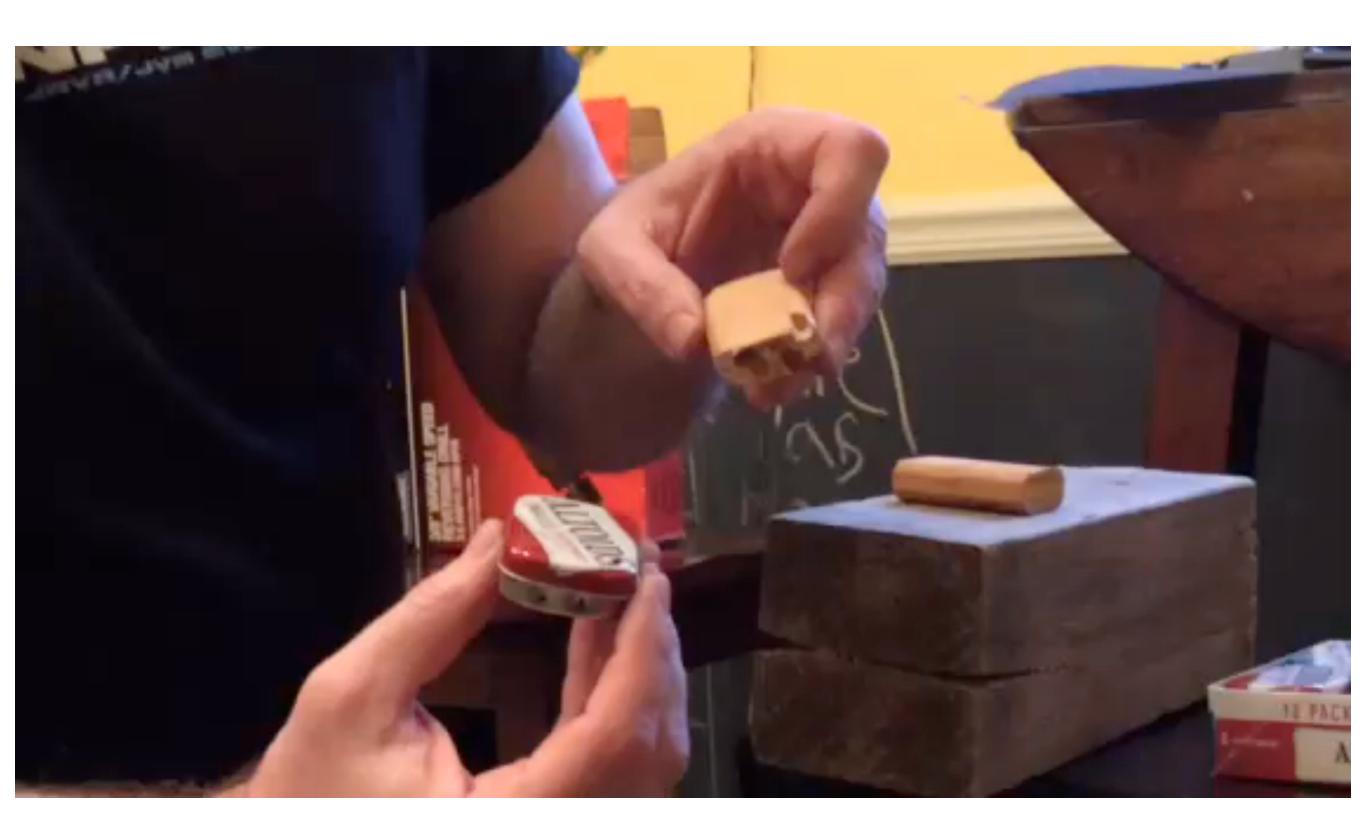


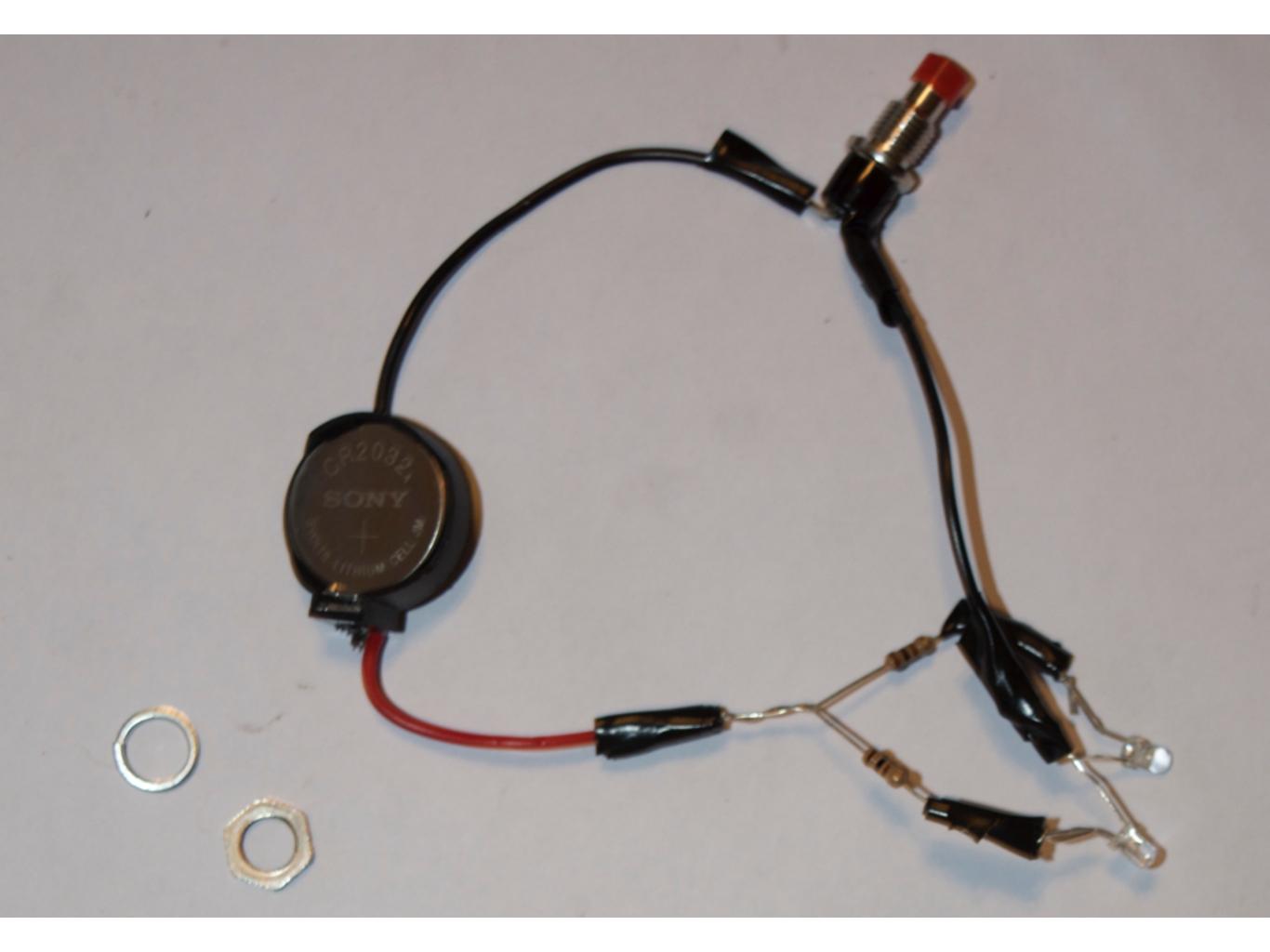


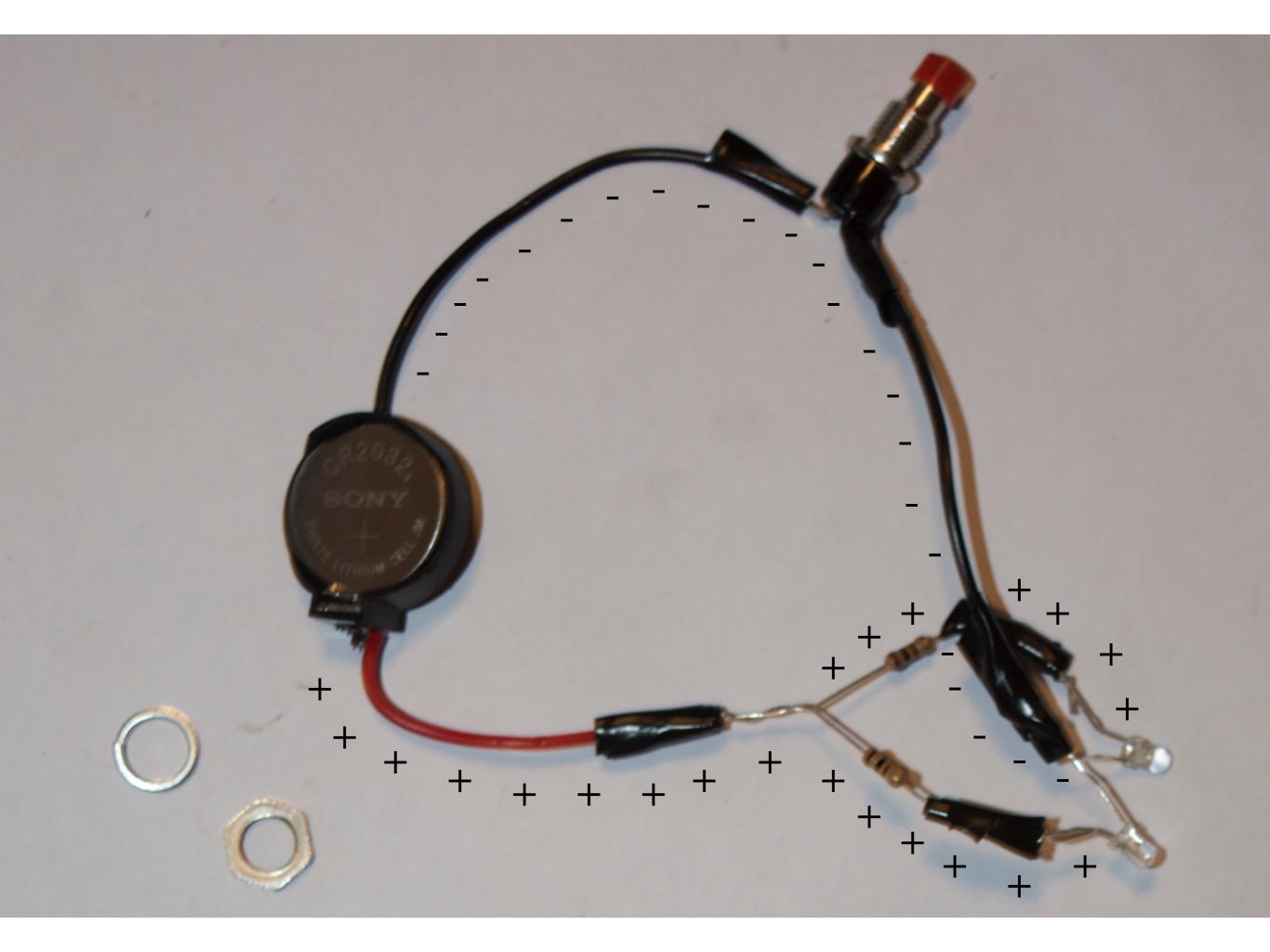

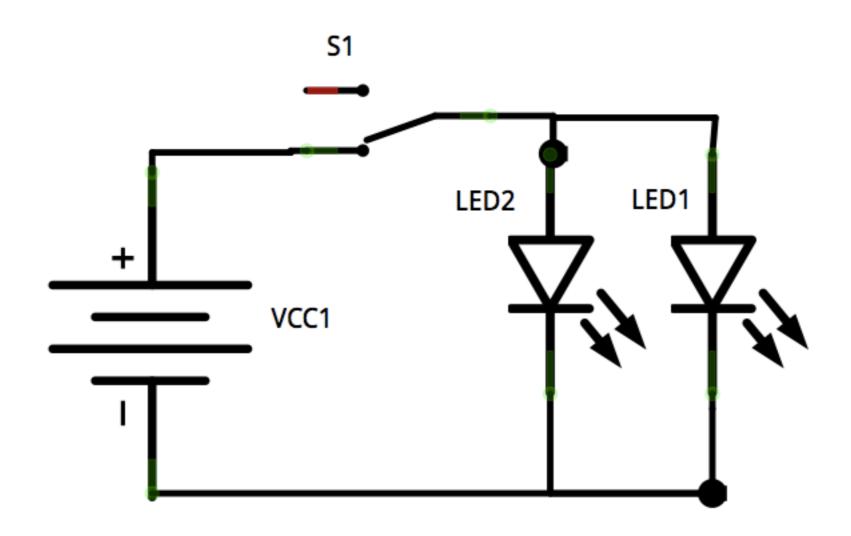

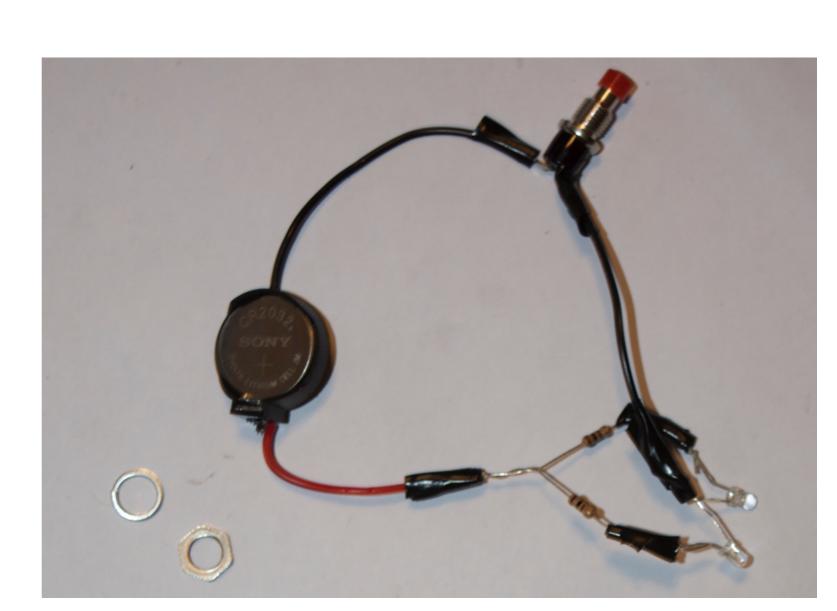- Connect coin holder black wire to button
- Connect black wire to button
- Twist negative LED wires together to form a M
- Connect black wire from button to middle of M
- Twist a resister to each positive LED wire
- Twist resisters together
- Connect Red wire from battery to twisted resisters
- Insert battery
- Press buttons



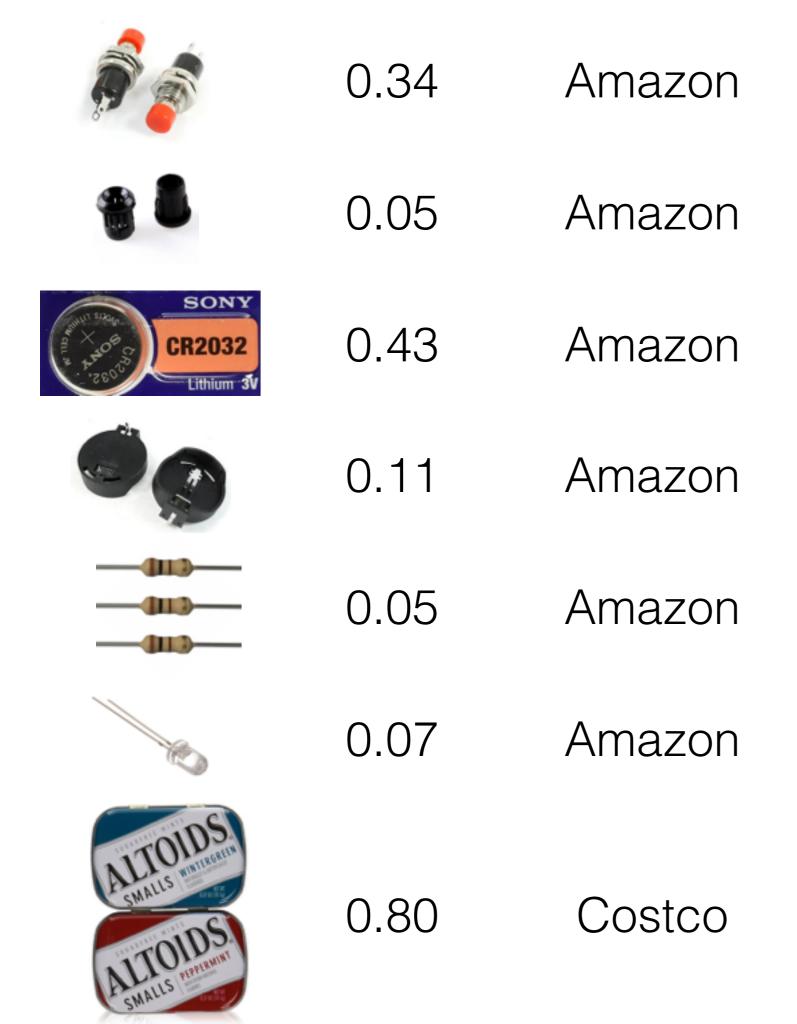

\$ 1.85

http://www.instructables.com/id/A-Better-Altoids-Smalls-LED-Flashlight/

