

# Electrical circuits

AST

PAGES 156–159

Complete this Concept Review so you can keep a record of what you have learned.


## Definitions

- An electrical circuit is \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

## Minimal components of an electrical circuit

Component	Function
	_____ _____ _____
Electrical resistance	_____ _____ _____
	_____ _____ _____

## Types of circuit

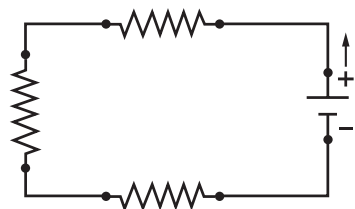Type of circuit	Definition	Example
	_____ _____ _____ _____	
	_____ _____ _____ _____	