Name:	Group:	Date:



Control and transformation of energy

AST		
PAGES 469-472		
Complete this Concept Review so you can keep a record of what		
you have learned.		

IJ	eti	nı	t.ı	n	ns

• A closed circuit is
• An open circuit is
Control is
The transformation of energy is

Different types of switches

Switch	Number of contacts that are opened or closed at a time	Number of possible paths for the electrons	Diagram
			→

Different types of switches

•	•	
•	 •	

Electrical components that are used to transform energy

Component	Form of energy obtained	