

Control and transformation of energy

Complete this concept review handout and keep it as a record of what you have learned.

Definitions

- A closed circuit is _____

- An open circuit is _____

- Control is _____

- The transformation of energy is _____

EST Different types of switches

Switch	Number of contacts that are opened or closed at a time	Number of possible paths for the electrons	Diagram

EST Different types of switches

- _____
- _____
- _____
- _____

Electrical components used to transform energy

Component	Form of energy obtained
_____	_____
_____	_____
_____	_____
_____	_____
_____	_____