

Electrical circuits

ST

 PAGES 156–159

Complete this Concept Review so you can keep a record of what you have learned.


Definitions

- An electrical circuit is _____

Minimal components of an electrical circuit

Component	Function
	_____ _____ _____
Electrical resistance	_____ _____ _____
	_____ _____ _____

Types of circuit

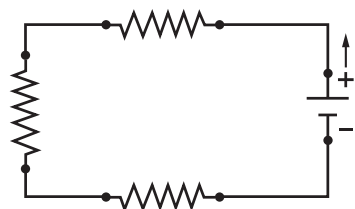Type of circuit	Definition	Example
	_____ _____ _____ _____	
	_____ _____ _____ _____	