

**Tech labs**

**TECH 15**

PROGRAMS: ST, EST, AST
LAB TYPE: Observation
CONCEPT: Control
STUDENT BOOK: Chapter 14, page 469
TOOLBOX: Pages 77 and 79

# Circuit control

**GOAL**

Observe several types of switches in electrical circuits.

**OBSERVATION CRITERIA**

1. What purpose do control components serve in electrical circuits?

---



---

2. What is the difference between an open circuit and a closed circuit?

---



---



---

3. Complete the table of switch types below with the following information:

- a) the number of contacts opened or closed at a time
- b) the number of paths that electrons may take
- c) the symbol for the switch

Type of switch	Number of contacts opened or closed at a time	Number of possible paths for electrons	Symbol
Single-pole, single-throw			
Single-pole, double-throw			
Double-pole, single-throw			
Double-pole, double-throw			

4. Draw the symbol for each of the circuit components below.

Electric cell ("battery")	Source of direct current (DC)	Electrical wire	Light bulb

**MATERIALS**

- 4 workstations, each with a different electrical circuit containing light bulbs

**PROCEDURE** 

**For each workstation:**

1. Make sure the DC power supply is working if the electrical circuit is powered by such a source.
2. Observe the number of possible switch positions that allow the bulb or bulbs to light up. Record your observations.
3. For each of these positions, observe the number of contacts that open or close simultaneously. To do this, count the number of light bulbs that light up or go out at the same time. Record your observations.
4. Study the electrical circuit. Draw the circuit diagram.
5. Repeat steps 1 to 4 at each workstation.
6. Put away the materials.

**OBSERVATIONS**

**Workstation 1**

1. How many switch positions allow one or more bulbs to light up? \_\_\_\_\_
2. How many bulbs light up or go out at the same time? \_\_\_\_\_
3. Draw the circuit diagram in the space below.

Name: \_\_\_\_\_ Group: \_\_\_\_\_ Date: \_\_\_\_\_

### Workstation 2

1. How many switch positions allow one or more bulbs to light up? \_\_\_\_\_
2. How many bulbs light up or go out at the same time? \_\_\_\_\_
3. Draw the circuit diagram in the space below.

### Workstation 3


1. How many switch positions allow one or more bulbs to light up? \_\_\_\_\_
2. How many bulbs light up or go out at the same time? \_\_\_\_\_
3. Draw the circuit diagram in the space below.

### Workstation 4

1. How many switch positions allow one or more bulbs to light up? \_\_\_\_\_
2. How many bulbs light up or go out at the same time? \_\_\_\_\_
3. Draw the circuit diagram in the space below.

### REFLECTING ON YOUR OBSERVATIONS

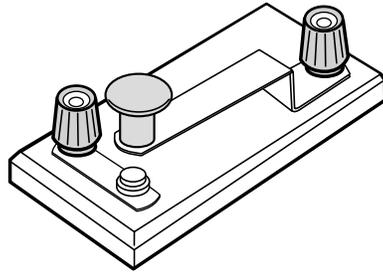1. According to your observations, what type of switch was installed in the circuit at:
  - a) Workstation 1? \_\_\_\_\_
  - b) Workstation 2? \_\_\_\_\_
  - c) Workstation 3? \_\_\_\_\_
  - d) Workstation 4? \_\_\_\_\_
2. Look at the illustration below. What type of switch is it?



- \_\_\_\_\_
3. Have your observations helped you understand the various types of switches? Explain your answer.  
\_\_\_\_\_  
\_\_\_\_\_
  4. How could you improve the protocol for this lab?  
\_\_\_\_\_  
\_\_\_\_\_