



[Visit Suncam.com for more courses](http://Suncam.com)

Continuing Education Course #357  
Transformers  
What Every Engineer Should Know

1. Referring to Figure 1 in the text, the turns ratio of a transformer is given by  $a = N_S / N_P$ .  
☐ a. true  
☐ b. false
2. In an ideal transformer power in = power out + losses, where losses are considered.  
☐ a. true  
☐ b. false
3. The efficiency of a transformer is given by  $1 - (\text{losses} / \text{power in})$ . Hint: this is an algebra problem!  
☐ a. true  
☐ b. false
4. The power factor of a transformer is given by  $\cos \theta = \text{watts} / \text{VA}$   
☐ a. true  
☐ b. false
5. K-Factor transformers  
☐ a. are designed to operate with non linear loads  
☐ b. have oversize windings and better ventilation to dissipate heat  
☐ c. have electrostatic shields to attenuate noise  
☐ d. all of the above
6. A three phase transformer has ONLY one flux path.  
☐ a. true  
☐ b. false
7. A phase displacement given by Dd10 is a delta to delta with a 60° lead.  
☐ a. true  
☐ b. false
8. Transformer regulation measures performance under load.  
☐ a. true  
☐ b. false
9. Referring to figure 2 in the text, if  $a = 4$ ,  $V_P = 460\text{v}$  and  $i_s = 10\text{amps}$ , what is  $V_S$ ?  
☐ a. 266 v  
☐ b. 115 v  
☐ c. 1840 v  
☐ d. none of the above

10. Referring to figure 2 in the text, if  $a = 4$ ,  $V_P = 460v$  and  $i_S = 10\text{amps}$ , what is  $i_P$ ?
- ☐ a. 4.3 amps
  - ☐ b. 40 amps
  - ☐ c. 2.5 amps
  - ☐ d. none of the above
11. In a three phase transformer with a delta primary, the line amps = phase amps x 1.73.
- ☐ a. true
  - ☐ b. false
12. In a three phase delta to delta transformer, if  $V_P = 600v$  and  $V_S = 120v$  and  $i_P$  is operating at 5 amps, what is the turns ratio?
- ☐ a. 3
  - ☐ b. 4
  - ☐ c. 5
  - ☐ d. None of the above
13. Continuing the problem from above, what is the value of  $i_S$ ?
- ☐ a. 1 amp
  - ☐ b. 4 amps
  - ☐ c. 5 amps
  - ☐ d. none of the above
14. Continuing the problem from question above, what is the operating KVA of the transformer? Hint: remember this is 3 phase!
- ☐ a. 3 KVA
  - ☐ b. 9 KVA
  - ☐ c. 5.2 KVA
  - ☐ d. none of the above
15. NEMA temperature code "A" represents a temperature rise of \_\_\_\_\_?
- ☐ a. 55°C
  - ☐ b. 80°C
  - ☐ c. 115°C
  - ☐ d. 150°C

[Purchase this course on Suncam.com](http://Suncam.com)